

## **Electronique ultra basse consommation solutions adiabatiques**

Hervé Fanet

CEA-Léti

[herve.fanet@cea.fr](mailto:herve.fanet@cea.fr)

# MINATEC on the scientific polygon



# Power aspects are nanoelectronics drivers

AMD motherboard with 1.1GHz 55 Watt Athlon Thunderbird



*Courtesy of AMD*


## Why less power?

## TODAY

- **access to powerful computation at any location**
  - restrictions on size, weight and power
  - small, but powerful batteries
- **increase in number of portables**
  - notebook, laptop
  - games
  - mobile phones
  - mobile DVD players
  - MP3 players
  - GPS

# Why less power?


# TOMORROW

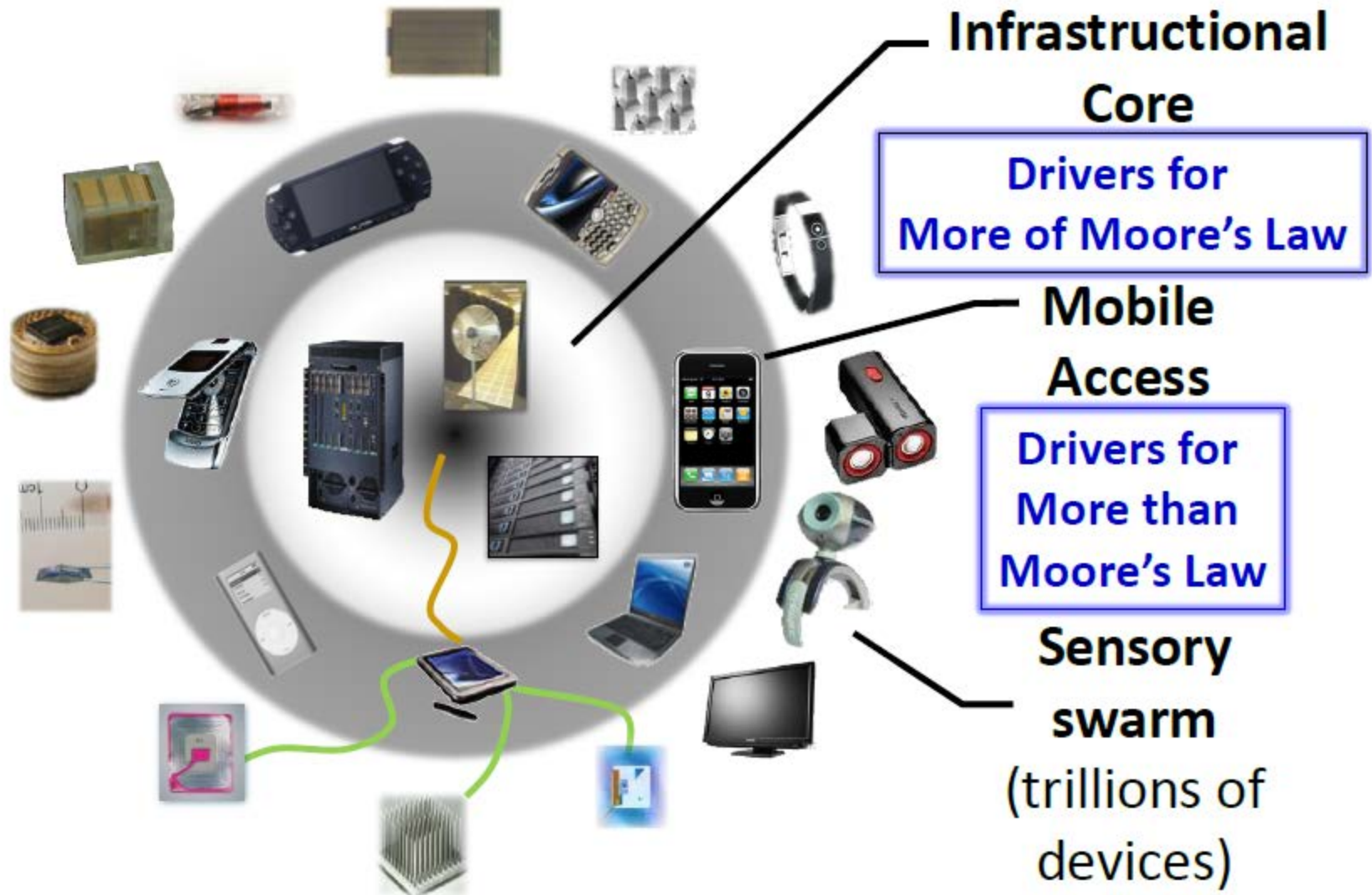

J. Rabaey, ASPDAC 2008

# Unfortunately the power density is not decreasing with CMOS scaling


## CMOS VOLTAGE SCALING

 

Source: P. Packan (Intel),  
2007 IEDM Short Course



## POWER DENSITY VS. GATE LENGTH

 

Source: B. Meyerson (IBM)  
Semico Conf., January 2004

- Power dissipation limitations are crucial for portable systems but also for supercomputers and all electronic applications
- How to solve this problem using nanocomponents ?
  - Decrease of capacitances and voltage...
  - Decrease of subthreshold current and tunnel effects...
  - New architectures....

# OUTLINE

- CMOS: what is necessary to know...
- Power dissipation: static power and dynamic power
- Power optimization at component and circuit level
- Power dissipation at architecture level
- Adiabatic and reversible computing




- **CMOS: what is necessary to know...**
  - **PMOS and NMOS**
  - **Inverters and logical functions**
  - **The global architecture**
- Power dissipation: static power and dynamic power
- Power optimization at component and circuit level
- Power dissipation at architecture level
- Adiabatic and reversible computing

# A basic function : the inverter

On if command is "0"


Off if command is "1"

 

On if command is "1"

Off if command is "0"


# A basic function : the inverter

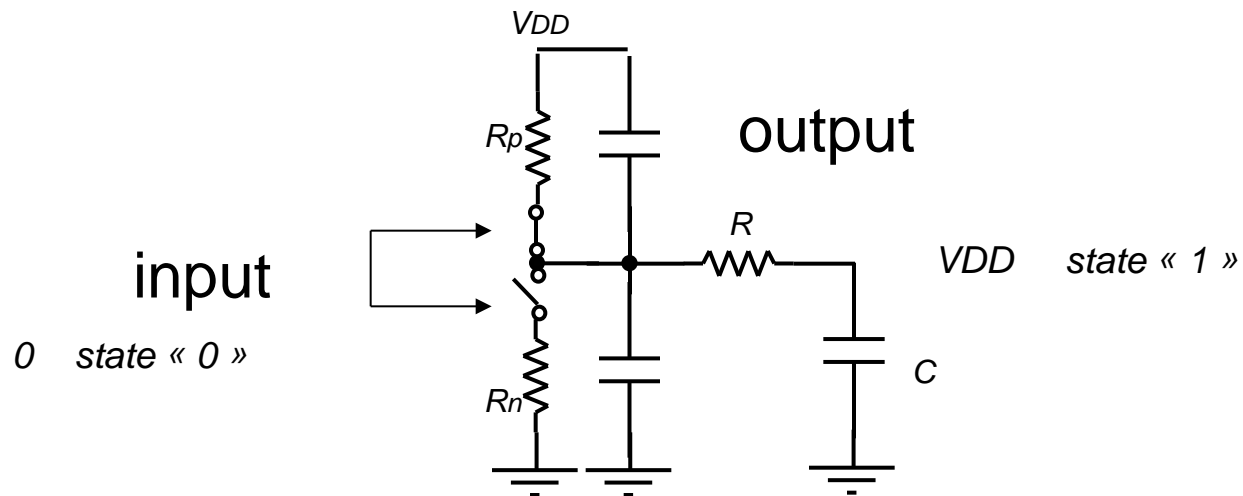

two different switches are necessary


# The NMOS transistor

under threshold

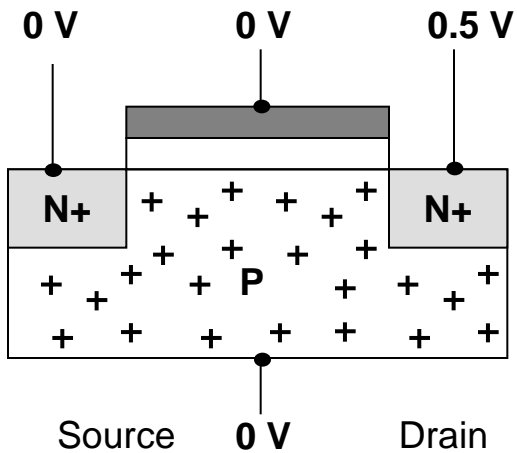


**MOSFET OFF**

above threshold

 

**MOSFET ON**

above threshold

 


**MOSFET ON and saturation**

# The PMOS transistor


below threshold

above threshold


above threshold

 



**MOSFET OFF**

 


**MOSFET ON**

 

**MOSFET ON and saturation**

  

 

L around 0,05 micron




W between 0.05 and 0.5 micron (except for analog or buffering)

$$I_{on} = WC'_{OX} v_{sat} (V_{GS} - V_T)$$

$v_{sat}$  saturation velocity of carriers in the conduction channel

$C'_{OX}$  capacitance per surface unit of the oxide layer


$V_T$  Threshold voltage

   



**multilevel of metallization**



# The microelectronic scaling principle

 

# The MOS transistor is a nanocomponent

  

# Basic FET model

- The  $I_{on}$  current (short channel)

$$I_{on} = WC'_{OX} v_{sat} (V_{GS} - V_T)$$

- The  $I_{off}$  current

$$I_{off} = Wk \exp^{\frac{-V_T}{nV_{th}}} \left( 1 - \exp^{-\frac{V_{DS}}{V_{th}}} \right)$$

*Strong effect of threshold voltage*

*Tunnel current in addition*

$$V_{th} = \frac{kT}{q}$$

The thermal voltage (25 mV at room temperature )

$$n = 1 + \frac{C_D}{C_n}$$


The body effect factor

$$C_n = WLC'_{OX}$$

$C_D$  depletion capacitance
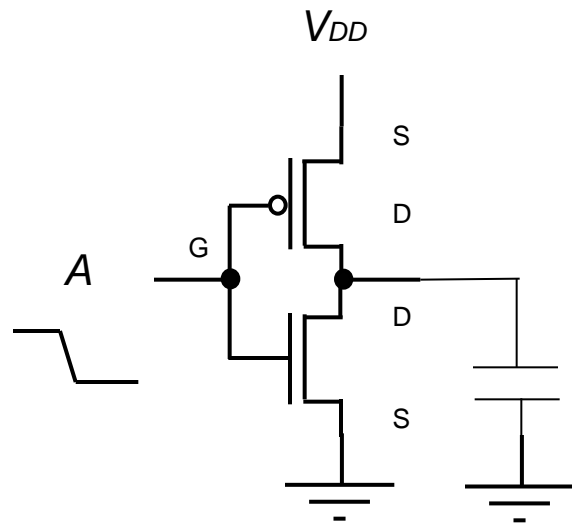
# Importance of $I_{on}$ et $I_{off}$

- $I_{off}$  defines leakage power consumption
- $I_{on}$  defines speed of the circuit




Charging time of the output capacitance

$$i = C \frac{\Delta V}{\Delta t}$$

Trade-off between speed and consumption

# The different modes

- Conventional and subthreshold modes

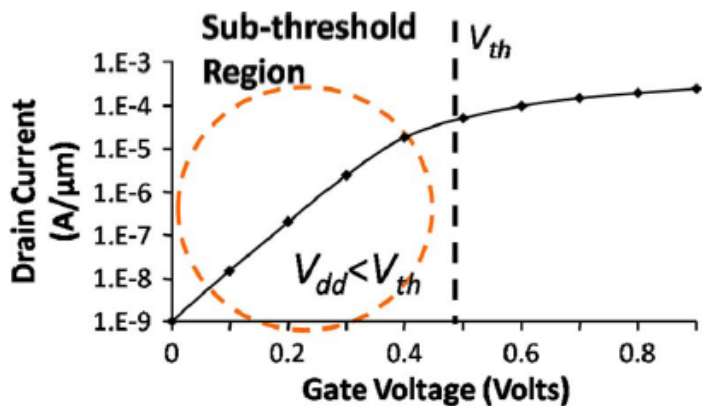


$$I_{sub} = n \cdot \mu \cdot \frac{C_n}{L^2} V_{th}^2 \exp^{\frac{V_{GS}-V_T}{nV_{th}}} \left( 1 - \exp^{-\frac{V_{DS}}{V_{th}}} \right)$$

$$V_{th} = \frac{kT}{q}$$

$$n = 1 + \frac{C_D}{C_n} \quad C_n = WLC'_{OX} \quad C_D \text{ capacitance of the depletion region}$$

- Linear and saturation modes

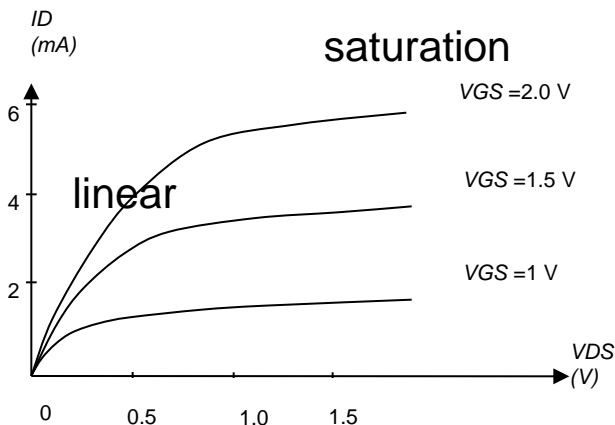


linear

$$I_{on} = \frac{W}{L} \mu \cdot C'_{OX} \left[ (V_{GS} - V_T) V_{DS} - \frac{1}{2} V_{DS}^2 \right]$$

saturation


$$I_{on} = \frac{1}{2} \frac{W}{L} \mu \cdot C'_{OX} (V_{GS} - V_T)^2 \quad \text{or} \quad I_{on} = WC'_{OX} v_{sat} (V_{GS} - V_T - V_{DSsat})$$

# An elementary function (NAND)

 




The inverter architecture

# A more complex cell: the half adder

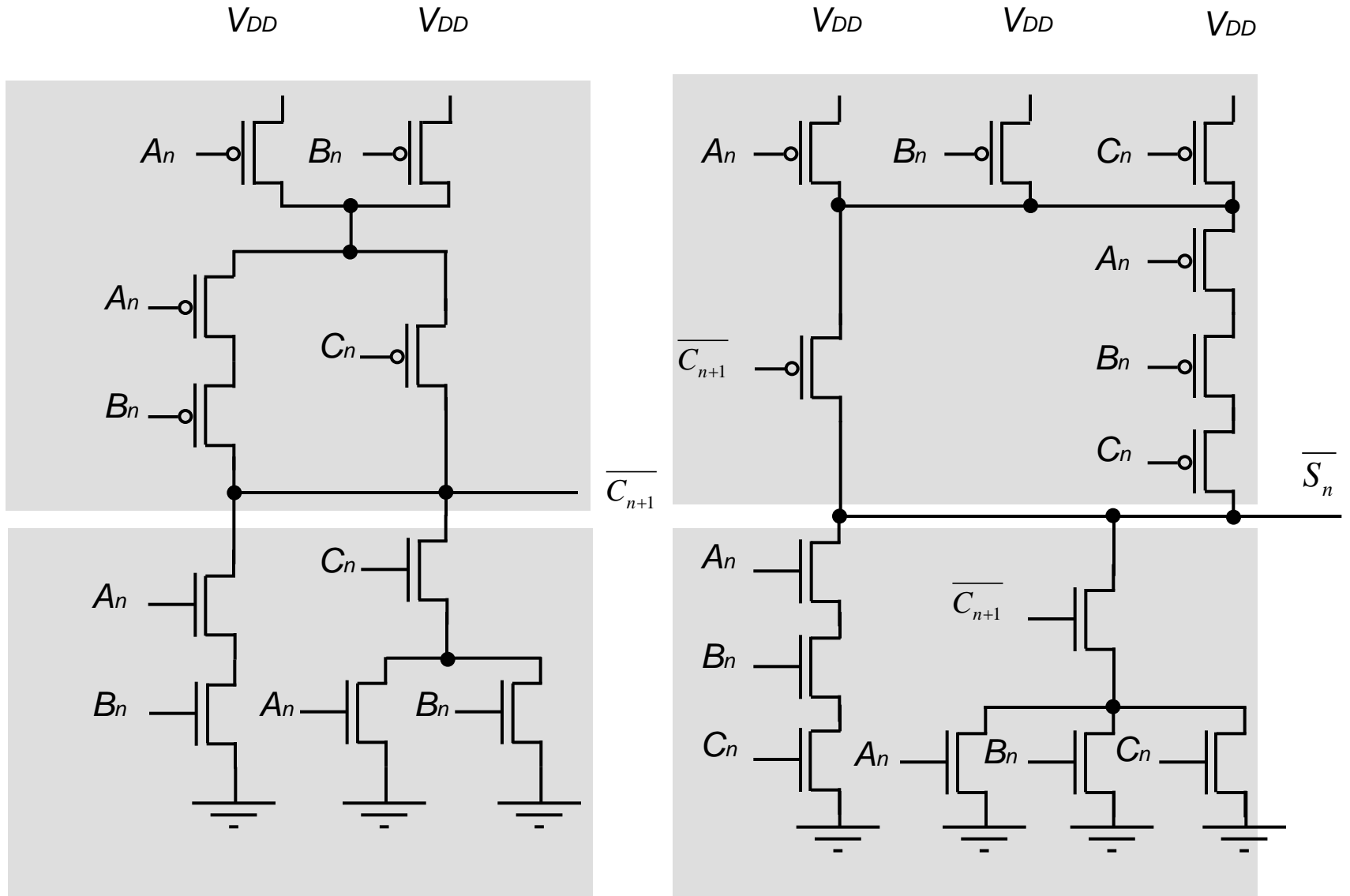


# Now systems are switch based systems


## Inverter is the basic element

   



**Logic**

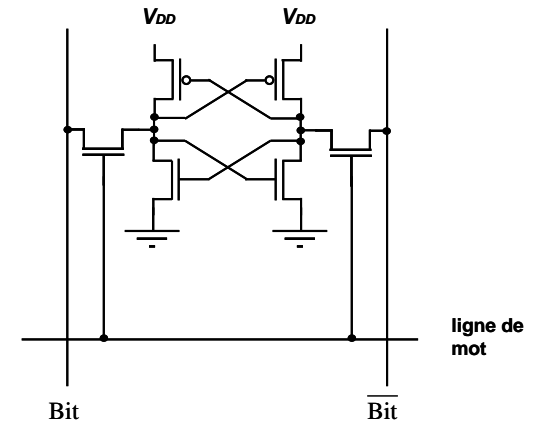

**Memory**

 




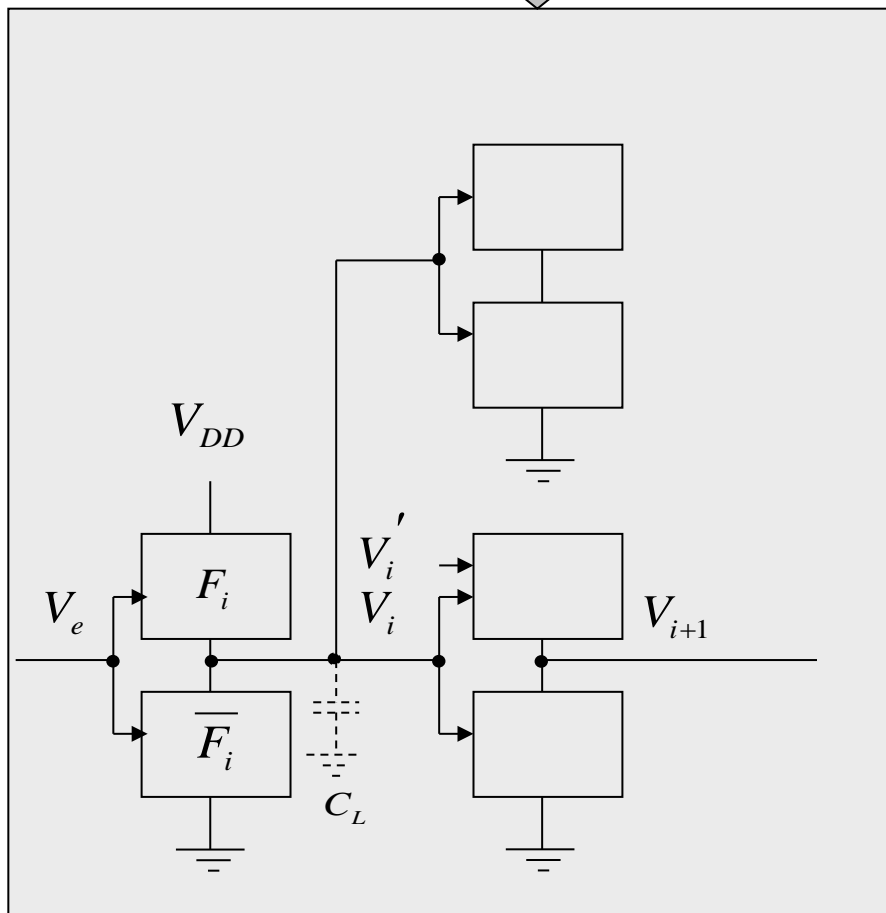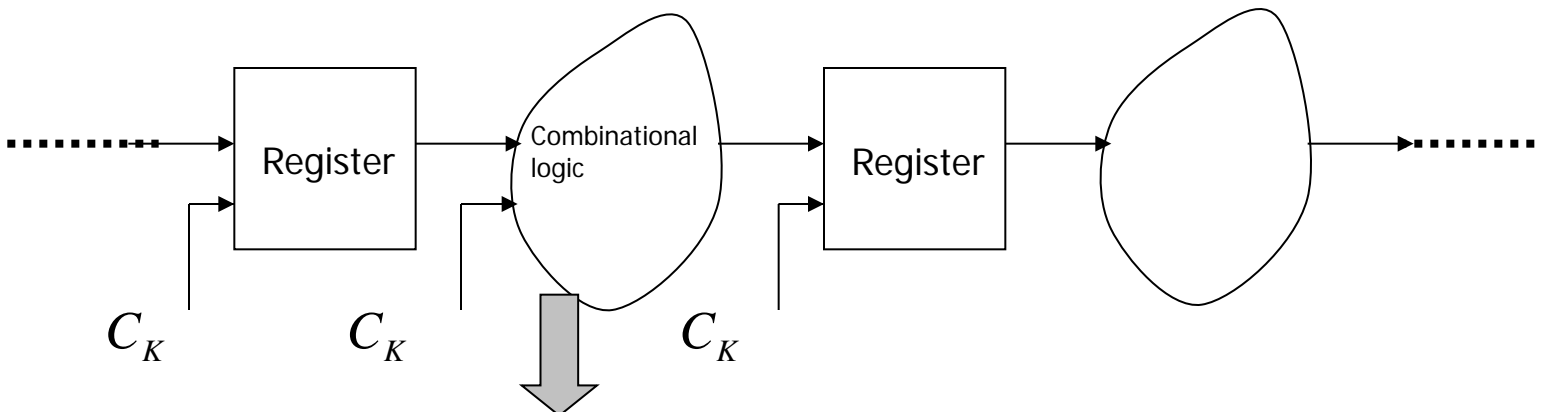

Complementary logic: no current is flowing if states do not change (except leakage)

Realization of a logic function is equivalent to close a serie of switches and to establish a conductive channel between supply and load

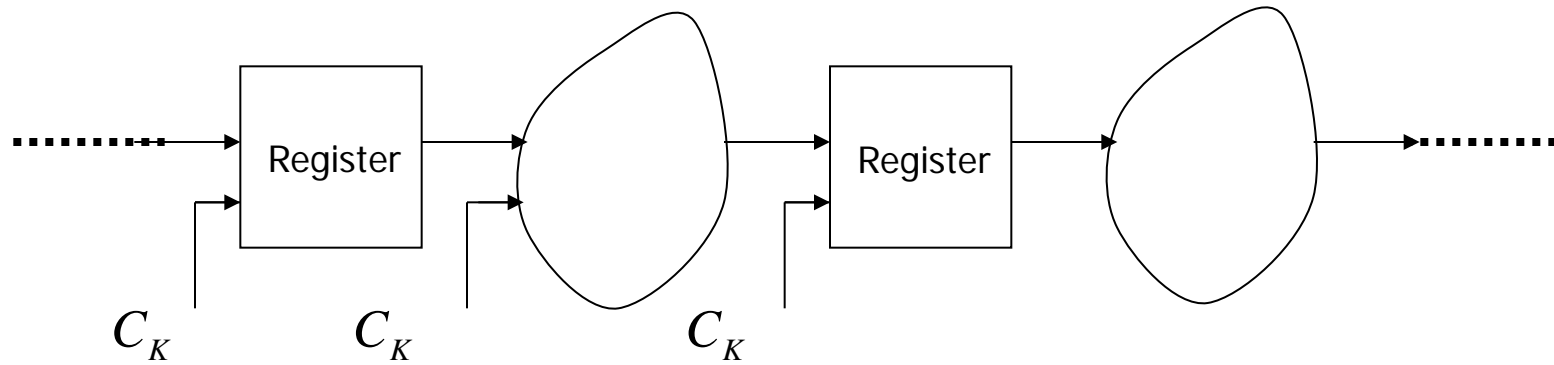**Logical depth  $L_D$**  is the maximum of gates in serie between two registers in the pipeline



**The activity rate  $\alpha$**  is the mean probability a gate change of state during the period T

- $N$  total number of gates
- $C_L$  mean load capacitance
- $f$  operating frequency
- $L_D$  logical depth
- $\alpha$  activity factor

$$f_{\max} = \frac{I_{on}}{L_D \cdot C_L \cdot V_{DD}}$$

$$P_{dyn} = \alpha \cdot N \cdot C_L \cdot V_{DD}^2 \cdot f$$

$$P_{stat} = N \cdot V_{DD} \cdot I_{off}$$

- CMOS: what is necessary to know...
- **Power dissipation: static power and dynamic power**
- Power optimization at component and circuit level
- Power dissipation at architecture level
- Adiabatic and reversible computing


$$P_{\text{total}} = P_{\text{active}} + P_{\text{standby}} =$$

$$= P_{\text{dyn}} + P_{\text{short}} + P_{\text{leak}}$$

The diagram shows the equation  $P_{\text{total}} = P_{\text{active}} + P_{\text{standby}} = P_{\text{dyn}} + P_{\text{short}} + P_{\text{leak}}$ . A horizontal curly brace is drawn under  $P_{\text{active}}$  and  $P_{\text{short}}$ , with a vertical line extending upwards from the center of the brace to the plus sign between  $P_{\text{active}}$  and  $P_{\text{standby}}$ . Another vertical line extends upwards from the plus sign between  $P_{\text{short}}$  and  $P_{\text{leak}}$  to the plus sign between  $P_{\text{active}}$  and  $P_{\text{standby}}$ .

$P_{\text{dyn}} = C V^2 \alpha f =$  dynamic power  
 = power dissipated due to charging and discharging (switching) of nodes  
 → **design & technology related**

 $P_{\text{short}} =$  short-circuit power  
 only during input transitions, there exists a short-circuit current from Vdd to ground → **design & technology related**



$$E_{\text{supply}} = V_{DD} \cdot \int_0^{\infty} i(t) dt = V_{DD} \cdot Q = CV_{DD}^2$$

$$Q = CV_{DD}$$

$$E_C = \frac{1}{2} CV_{DD}^2$$

Dissipated energy



$$E_R = \frac{1}{2} CV_{DD}^2$$

Dissipation independent of  $R$  ( switch resistance) and duration of operation

$R$  may change during transition

Only true if  $V_{DD}$  constant (conventional logic)

# Leakage power and dynamic power

  

$$P_{leak} = I_0 V_{DD} \exp^{-\frac{V_T}{nV_{th}}} + V_{DD} I_t$$

$$P_{dyn} = \alpha f C V_{DD}^2$$

$$n = 1 + \frac{C_D}{C_n} \geq 1$$

# How to reduce leakage power

The subthreshold current

The tunnel current

$$P_{leak} = N \cdot I_0 V_{DD} \exp^{\frac{V_T}{nV_{th}}} + N \cdot V_{DD} I_t$$

To use sleep modes  
for circuit or blocks

To decrease  $n$


To increase  
threshold voltage

To eliminate tunnel  
effects

# How to reduce dynamic power

$$P_{dyn} = \alpha N f C V_{DD}^2$$


To increase  
parallelism

 

To reduce  
interconnect




To decrease  
supply voltage

 



# Is it possible to reduce the operating frequency ?

## Parallelism is an efficient solution

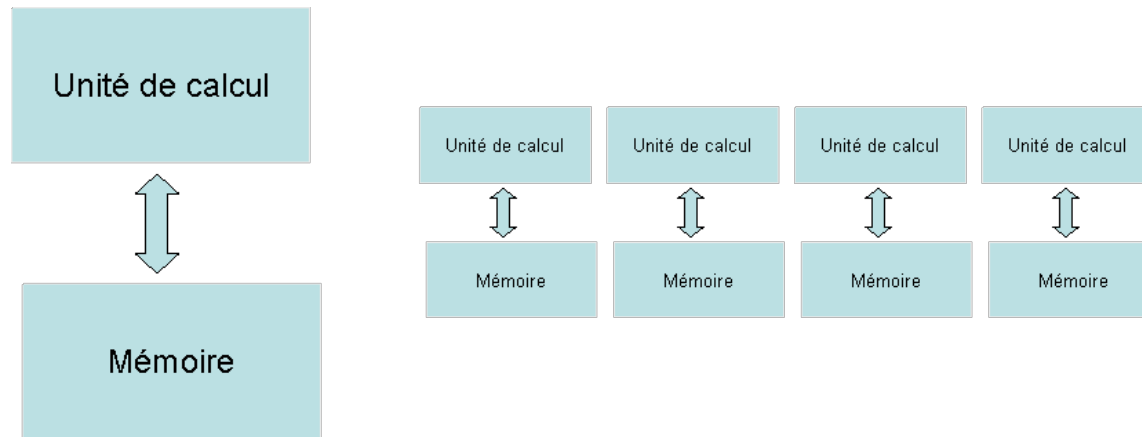


$$P = NfCV^2$$

$$P = 4N \frac{f}{4} \frac{C}{4} \left(\frac{V}{4}\right)^2$$

Today advanced architectures use parallelism but parallelism has limitations

## Intel's Nehalem-EX Processor

 


- 45nm process with Hi-K / Metal Gate
- 8 cores, 16 threads
- 24MB L3 cache
- 4 QPI links
- 2.3B transistors
- 130W TDP

- Power reduction techniques:
  - Operate at the lowest possible voltage (0.85V cores, 0.9V cache)
  - Clock and power gate inactive cores and cache slices
  - Multiple voltage and frequency domains, on-die power management unit
  - Extensive use of long channel devices on paths with timing slack


# Is it possible to reduce the capacitance ?

	2009	2012	2020
<b>Métal 1</b>			
C in pF/cm	2	1,8	1,3
RC in ns/mm	1	5	50
<b>Medium</b>			
C in pF/cm	2	1,8	1,3
RC in ns/cm	1	5	50
<b>Global</b>			
C en pF/cm	2,3	2	1,4
RC en ps/cm	11	10	7

# Interconnections and load capacitances

 
 
# Is it possible to reduce the supply voltage ?




It is not easy to reduce supply voltage...

- CMOS: what is necessary to know
- Power dissipation: static power and dynamic power
- **Power optimization at component and circuit level**
  - **Applications and metrics**
  - **How to reduce supply voltage**
  - **Interest of steep slope devices**
- Power dissipation at architecture level
- Adiabatic and reversible computing
 
# How to reduce supply voltage, the limits

- 1 Trade-off speed-dissipation
- 2 variability and design constraints
- 3 Cascadability of gates
- 4 Thermodynamical limit



# 1 The trade-off power-speed

- The power-delay product assigns equal weight to the power and to the delay of a circuit:

$$\text{Power} \cdot \text{Delay} = P_{\text{dyn}} \cdot \tau$$

- For circuits for which power has a higher priority than speed, we might give a higher weight to the power than to the delay and the metric becomes:

$$\text{Power} \cdot \text{Energy} = P_{\text{dyn}}^2 \cdot \tau$$

- For high-speed circuits we might give more weight to the delay instead of to the power. Then the metric becomes equal to the energy-delay product:

$$\text{Energy} \cdot \text{Delay} = P_{\text{dyn}} \cdot \tau^2$$



# The trade-off power-speed in conventional mode

- very important performance metric is: **power-delay product**

- **Power =  $C V^2 \alpha f$**

- **delay =  $2CV/\beta(V-V_T)^2$**

$$Q = i t = C V$$

$$t = CV/i \quad \text{and} \quad i = \beta/2 \cdot (V-V_T)^2$$

- to reduce both power and delay, **C** needs to be reduced

- power-delay product:  **$\tau D = bV^3/(V-V_T)^2$**

- optimum at  $\delta\tau D/\delta V = 0 \rightarrow$

$$V = 3V_T$$





# The trade-off power-speed in subthreshold mode

$$\tau \approx \frac{V_{DD}}{(V_{DD} - V_T)^{3/2}}$$



Trade-off speed consumption

  

*Dreslinsky et al proceeding IEEE 2010*

To reduce power dissipation low frequency operation is necessary and supply voltage around 0,35 V is optimum for CMOS

- very robust operation with large noise margins
- can operate at  $V_{dd}$  below sum of threshold voltages
- → sub-threshold (logic) operation
- 45nm CMOS (nominal supply: 1.1V) can still operate 80mV
- but, then, only at very low frequencies and with a huge spread:
  - 30mV spread in  $V_t$  may lead to 9 times difference in speed, because of huge (leakage) current difference

# The minimum energy operation

B H Calhoun and A Chandrakasan: Characterizing and modeling minimum energy operation for subthreshold circuits

$$I_{sub} = I_0 e^{\frac{V_{GS} - V_T}{nV_{th}}} \quad t_d = \frac{CV_{DD}}{I_0 e^{\frac{V_{GS} - V_T}{nV_{th}}}}$$

$$E = \alpha \cdot CV_{DD}^2 + WL_D CV_{DD}^2 e^{\frac{V_{DD}}{nV_{th}}}$$

$$V_{DDopt} = nV_{th} (2 - \text{lambertW}(\beta))$$


$$\beta = \frac{-2C\alpha}{WCL_D} e^2$$

$$\beta = \frac{-2C\alpha}{WCL_D} e^2 \geq -e^{-1}$$

$$V_{Topt} = V_{DDopt} - nV_{th} \cdot \ln\left(\frac{fCL_D V_{DDopt}}{I_0}\right)$$

$\text{lambertW}(x)$  is the solution of  $we^w = x$
 
# Decrease of elementary switching energy



Yes but increase of operating gates and variability effects

## 2 Variability and design constraints

Global analysis necessary including variability and power consumption analysis

$$\tau = k \frac{V_{DD}}{(V_{DD} - V_T)^\eta}$$

$$\eta \approx 1.3$$

$$\Delta\tau = \frac{\tau(V_T + \Delta V_{T\max})}{\tau(V_T)}$$


$$\Delta V_{T\max} = \frac{A}{\sqrt{LW}}$$

**Law of Pelgrom**

$$V_{DD\min} = V_T + (1 + \gamma)\Delta V_{T\max}$$

$$\gamma = \frac{1}{\Delta\tau^{1/\eta} - 1}$$

# Variability and technologies

 



- Dopant fluctuations is dominant component for bulk planar
- Finfet has LER and L\_Gate variations primarily
- ETSOI has L\_Gate and BOX charge effects

# 3 The cascadability of gates

Gupta 2010 proceeding IEEE

The subthreshold regime
  
$$I = \mu_n V_T^2 e^{\frac{V_{GS} - V_T}{nV_{th}}} \left[ 1 - e^{-\frac{V_{DS}}{mV_{th}}} \right]$$



A:  $(V_{i1}, V_{o1})$ ; B:  $(V_{o2}, V_{i2})$ ; C:  $(V_{i3}, V_{o3})$ ;  
 $S_1$ :  $(V_{o}, V_i)$ ;  $S_0$ :  $(V_i, V_o)$

$$n = 1 + \frac{C_D}{C_n}$$

$$V_{th} = \frac{kT}{e}$$

$$m \approx 1$$

The two stable points are the same if

$$V_{DD\min} = 2n \frac{kT}{e} \text{Ln} \left( 1 + \frac{m}{n} \right)$$



# 4 The fundamental limits

- Boltzmann + Shannon : Minimum switching energy

$$E \succ k_B T \ln 2$$

- Heisenberg : Minimum channel length

$$L \succ \frac{\hbar}{\sqrt{2mE}}$$

- With tunnel effect (Zhirnov-Cavin)

$$E \succ k_B T \ln 2 + \frac{\hbar^2 (\ln 2)^2}{8mL^2}$$

# What is the minimum value of VDD- summary

- Trade-off Speed-Power

200-700 mV (less if low perf)

- Variability and design constraints

100-300 mV


- Cascability of devices

20-50 mV



- For very low voltage fundamental limits

Below 20 mV towards 2 mV

# Interest of steep slope devices ?

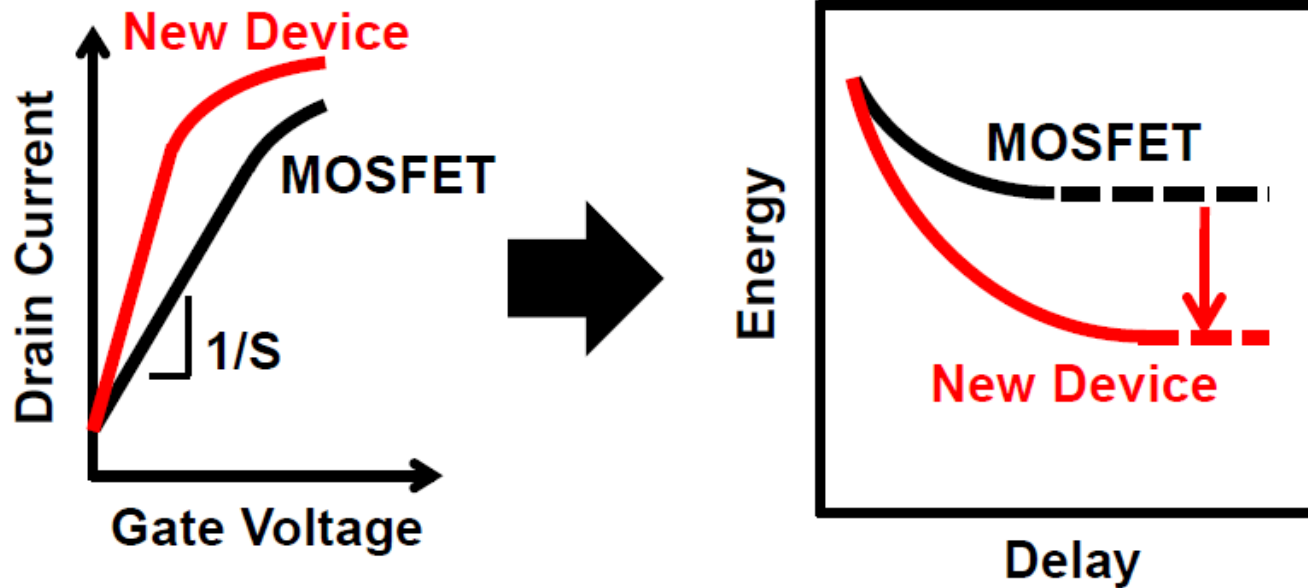

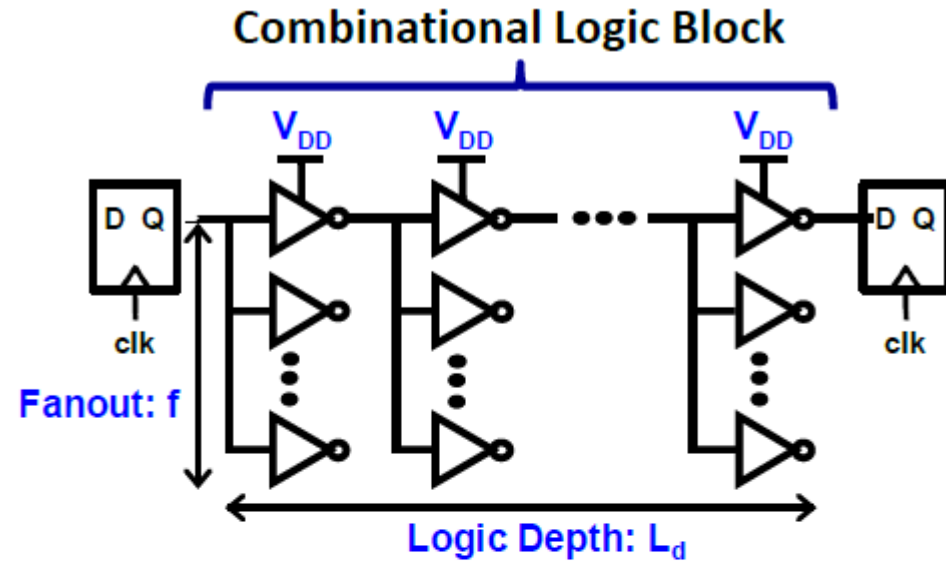 Prof. Tsu-Jae King Liu  
Workshop on Zero power technologies for Autonomous Smart Systems



$$E_{\text{total}} = \underbrace{\alpha L_d f C V_{DD}^2}_{\text{Active Energy}} \left[ 1 + \underbrace{(L_d f / 2\alpha) (I_{\text{OFF}} / I_{\text{ON}})}_{\text{Passive Energy}} \right]$$



$$t_{\text{delay}} = L_d f C V_{DD} / (2 I_{\text{ON}})$$

- A lower limit in E/op exists due to transistor OFF-state leakage.



$\alpha$ : Activity Factor     $L_d$ : Logic Depth     $f$ : Fanout     $C$ : Capacitance per Stage

B. Calhoun *et al.*, *IEEE J. Solid State Circuits*, Vol. 50, pp. 1778-1786, 2005
  
# Interest of steep slope devices/ the Tunnel FET



$$I_D \propto \exp(qV_{GS}/nkT)$$

 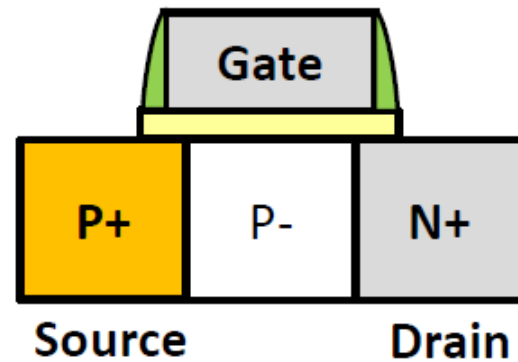



$$I_D = AE_S \exp(-B/E_S)$$

( $E_S$  = electric field)

# Interest of steep slope devices/ the nanomechanical relay



- Zero off-state leakage  
→ zero leakage energy
- Abrupt switching behavior  
→ allows for aggressive  $V_{DD}$  scaling  
(ultra-low dynamic energy)

## 3-Terminal Switch

  

Prof. Tsu-Jae King Liu  
Workshop on Zero power technologies for Autonomous Smart Systems

# Nano-Electro-Mechanical (NEM) Switch

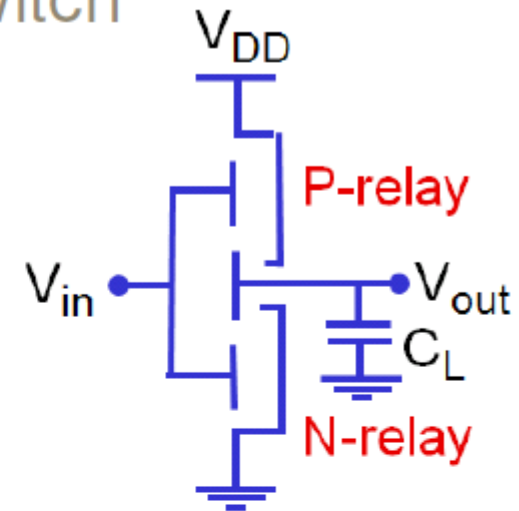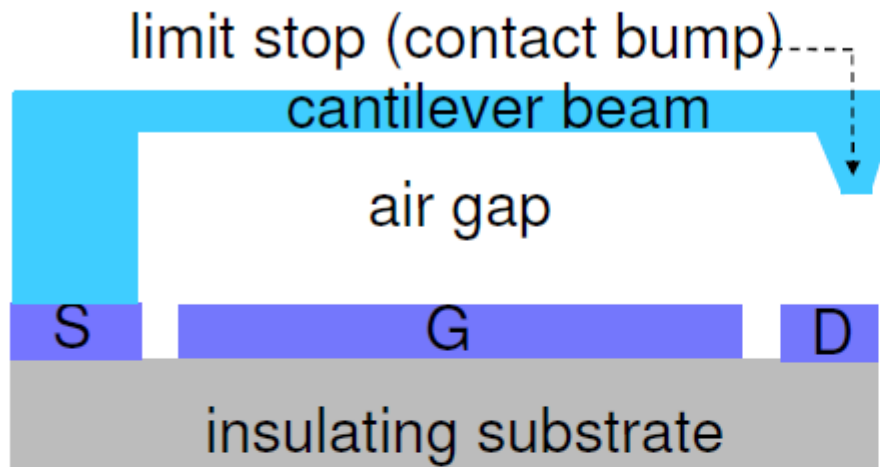

$V_{DD}$	1.5 V
$V_{pi}$	1 V
$g_0, h$	10 nm
L	~250 nm
W	100 nm







## Simple NEM relay

Static Power	'Zero'
Switching Delay	1 nsec (Si)
Switching Energy	0.08 fJ (Si)
Inverter Area	0.03 $\mu\text{m}^2$



K. Akarvardar, D. Elata, R. Parsa, G. C. Wan, K. Yoo, J. Provine, P. Peumans, R. T. Howe, H.-S. P. Wong, "Design Considerations for Complementary Nanoelectromechanical Logic Gates," *IEEE International Electron Devices Meeting (IEDM)*, p. 299, December 10 – 12, Washington, D.C., 2007.

# Nanoelectromechanical (NEM) Relay

   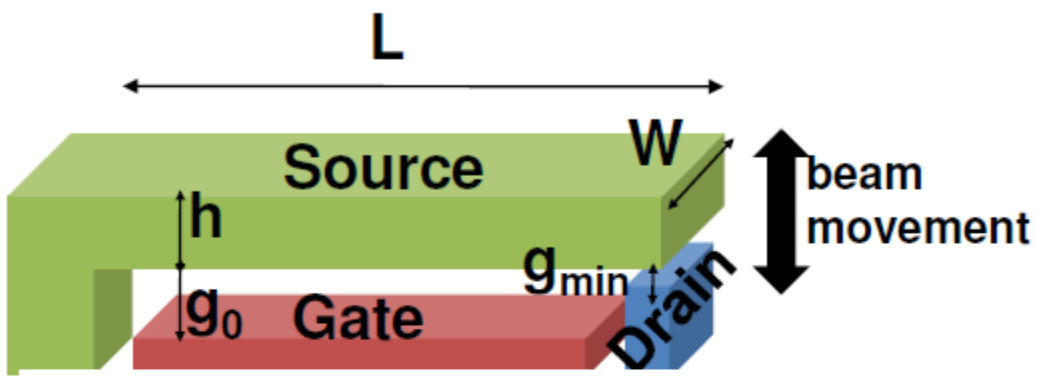

S. Chong ...H.-S. P. Wong, "Nanoelectromechanical (NEM) Relays Integrated with CMOS SRAM for Improved Stability and Low Leakage," *ICCAD 2009*.



- **NEM switches have several potential advantages compared with nanoscale CMOS transistors:**


- low power supply (100 mV)
- high on current
- 'zero' leakage
- 'infinite' subthreshold slope
- high temperature operation
- radiation-hard operation
- compatible with other substrates ... glass, plastics

- **... and “just a few” problems:**

- reliability (stiction, contact degradation, wear, ...)
- slow speed

- CMOS: what is necessary to know...
- Power dissipation: static power and dynamic power
- Power optimization at component and circuit level
- **Power dissipation at architecture level**
- Adiabatic and reversible computing


## HP, LOP, LSTP for Logic CMOS

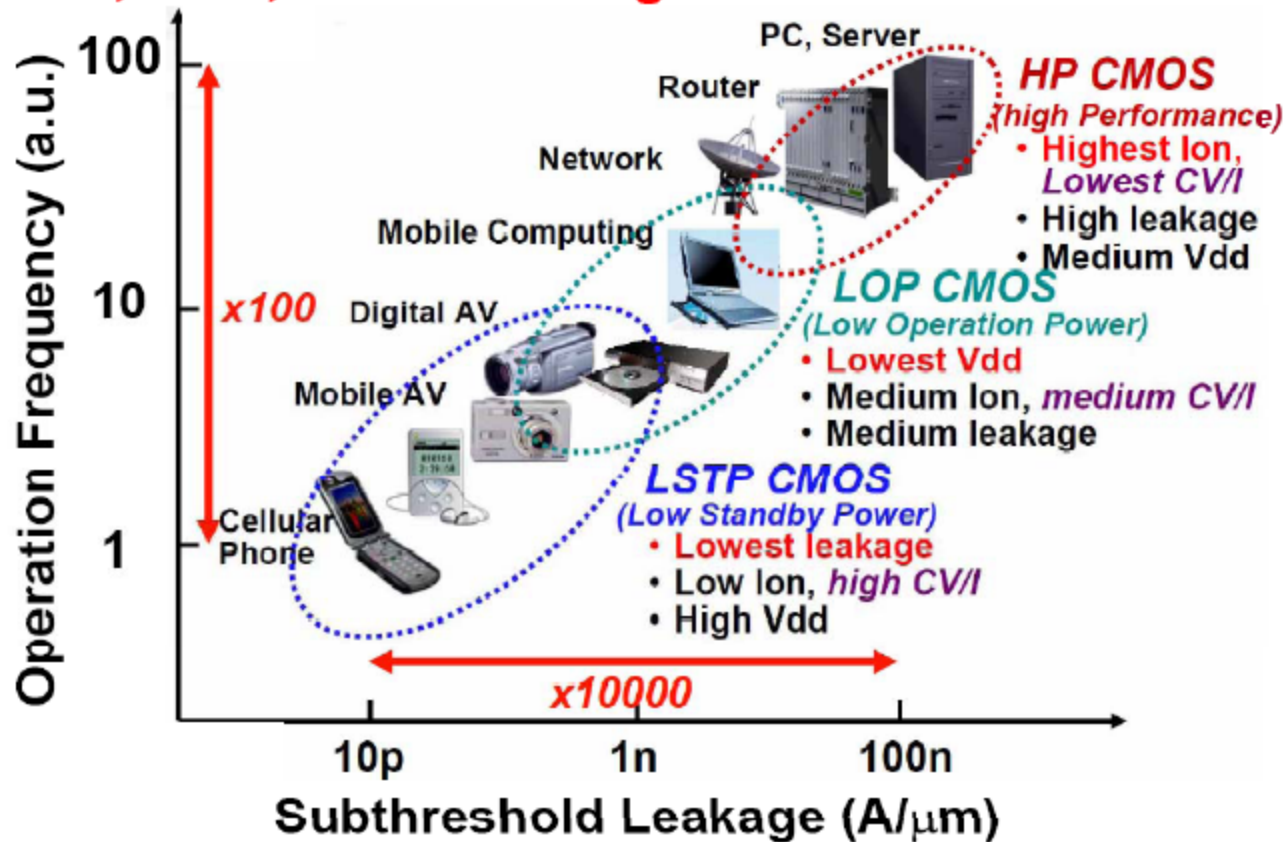

Source: 2007 ITRS Winter Public Conf.

1

# Trade-off flexibility-power

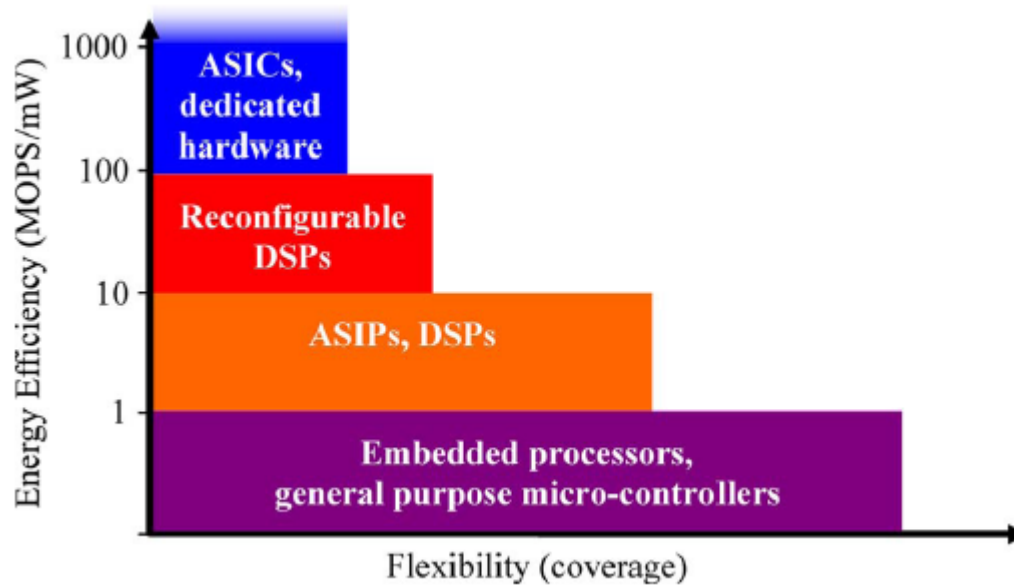


**With an ASIC a factor 100 is possible for power reduction**

# Optimization of voltage and frequency

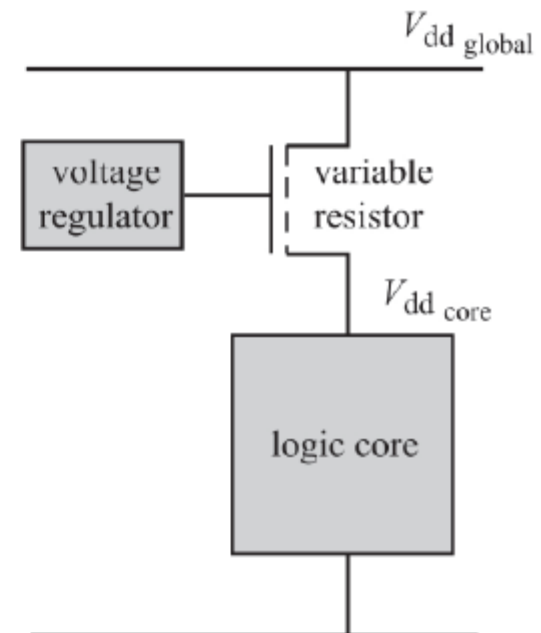
## dynamic voltage and frequency scaling (DVFS)

- dynamically adjusting the voltage to the performance needs
- requires on- or off-chip voltage regulator
- varying the resistance of a big transistor between the core and the supply voltage
- but power reduces only linearly with the  $V_{dd_{core}}$  instead of quadratically, since part of the power saving in the core is now consumed in the variable resistor.


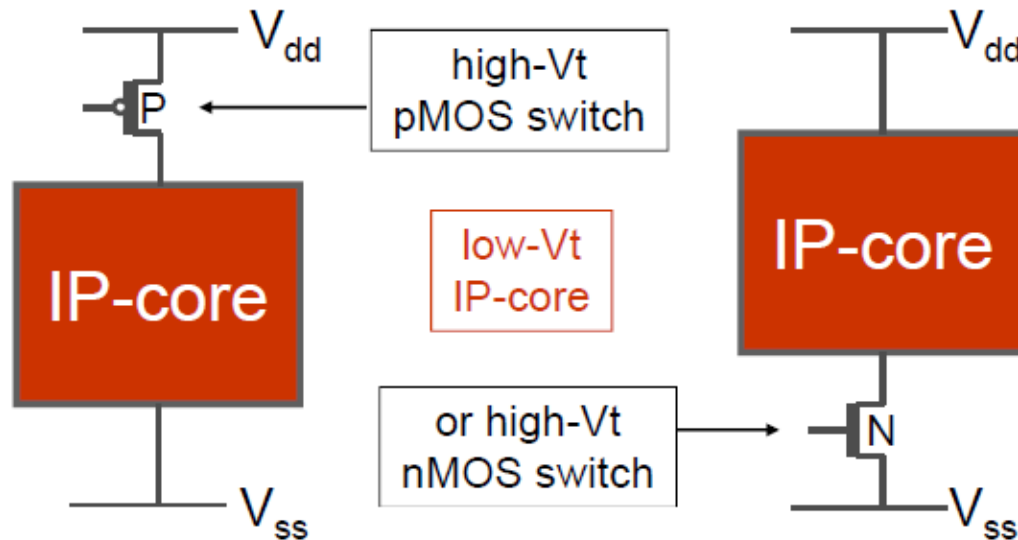
# Optimization of Threshold voltages

- multiple  $V_t$  concept: **HVt power switches**
  - switch off **low- $V_t$  core** with **high- $V_t$  transistors** (high- $V_t$  power switches)
  - disadvantages: core flip-flops lose their states → multi-supply flip-flops



# Optimization of SRAMS

- **reduce supply voltage of memory array in standby mode**
  - memory operation is very critical wrt supply voltage
  - but in standby mode only data retention is required
  - can be done at (somewhat) lower voltages
  - use of 7 or 8 transistor cells may also support low-standby voltage
- **use high-Vt transistors in the memory cells**
  - most transistors of an SoC are in the memory (often > 80%)
  - so, memories relatively contribute most to the standby power
  - HVt transistors in the cells will greatly reduce standby power

# A low power processor

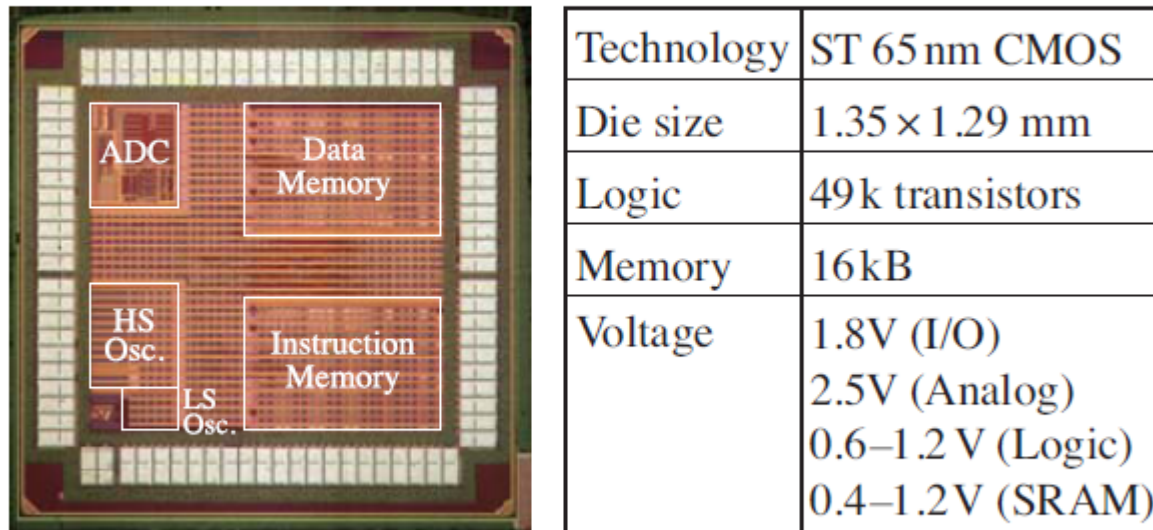


Fig. 5. Chip photomicrograph and design statistics.



# A low power processor


 


Fig. 7. Breakdown of digital power consumption by module at 0.6 V (SRAM array voltage 0.4 V).


# A low power SOC

 


H.264 encoder,

65nm low-power technology,

1.0V, down to  
0.57nJ/pixel

 


$V_{DD}=1.0V$   
Total power = 2.68mW

 


$V_{DD}=0.6V$   
Total power = 648μW

 - Dynamic (Logic)
- Leakage (Logic)
- Dynamic (Memory)
- Leakage (Memory)



$V_{DD}=0.48V$   
Total power = 312μW
 
# Example of an autonomous sensor for energy efficiency in building



# Example of an autonomous sensor for energy efficiency in building


 


Figure 22 : Current consumption repartition in function of demonstrator operating mode

- **CMOS: what is necessary to know...**
- Power dissipation: static power and dynamic power
- Power optimization at component and circuit level
- Power dissipation at architecture level
- **Adiabatic and reversible computing**

<b>Adiabatic logic</b>	<b>Reversible logic</b>
<p data-bbox="100 396 904 605">How to charge and discharge a capacitance with minimum energy dissipation</p> <p data-bbox="100 729 823 782"><i>To work at constant current</i></p>	<p data-bbox="981 396 1765 605">How to take into account Landauer principle in order to minimize energy dissipation</p> <p data-bbox="981 729 1680 782"><i>To use only reversible logic</i></p>

# Information and heat dissipation

 



$$\Delta Q = T\Delta S$$

$$\Delta H = \Delta \left( - \sum_i p_i \ln_2 p_i \right)$$


$$\Delta S = k\Delta H$$

# Information and heat dissipation

IN		OUT	
0	0	0	0
0	1	1	0
1	0	1	0
1	1	1	1

  



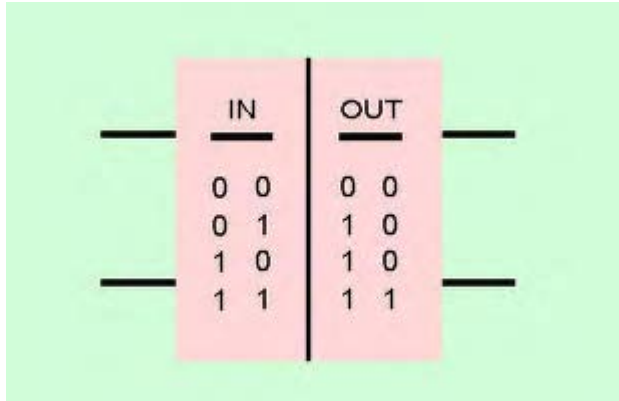

$$H_{in} = - \sum_{states} p_{state} \log_2 p_{state} = -4 \times \frac{1}{4} \log_2 \frac{1}{4} = 2$$

$$H_{out} = -2 \times \frac{1}{4} \log_2 \frac{1}{4} - \frac{1}{2} \log_2 \frac{1}{2} = \frac{3}{2}$$


**An example of non reversible gate**

**Impossible to guess inputs from outputs**

Input			Output		
C <sub>1</sub>	C <sub>2</sub>	T	C <sub>1</sub>	C <sub>2</sub>	T
0	0	0	0	0	0
0	0	1	0	0	1
0	1	0	0	1	0
0	1	1	0	1	1
1	0	0	1	0	0
1	0	1	1	0	1
1	1	0	1	1	1
1	1	1	1	1	0

**An example of a reversible gate: the Toffoli Gate**


# The adiabatic charge of a capacitance

 


Not an abrupt variation but a linear variation is applied to the capacitor

If  $RC$  is small compared to the duration  $T$  of the ramp, charge-discharge currents and Joule dissipation are small

**$RC/T$  small**

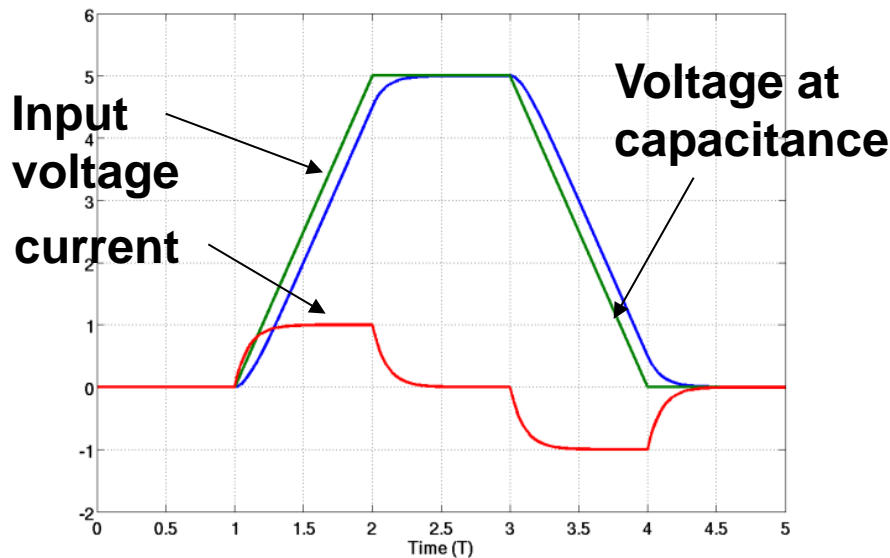

**$RC/T$  very small**

 


# 1) Conventional

$$E_{\text{alim}} = V_{DD} \cdot \int_0^{\infty} i(t) dt = V_{DD} \cdot Q = CV_{DD}^2$$

$$Q = CV_{DD}$$

$$E_C = \frac{1}{2} CV_{DD}^2$$

$$E_R = \frac{1}{2} CV_{DD}^2$$

 

*Only true if  $V_{DD}$  does not vary with time*

# 2) Adiabatic


$$Q = CV_{DD}$$

$$i = \frac{Q}{T}$$

$$E_R = Ri^2T = R \frac{Q^2}{T^2} T = \frac{RC}{T} CV_{DD}^2$$

*Only true if  $i$  does not vary with time*


## Charge of CL

 

$$E_{dissipée} = \frac{RC_L}{T} C_L V_{DD}^2$$

$$i = \frac{C_L \cdot V_{DD}}{T}$$

## Discharge of CL

 

- Charge is at constant current during T and voltage at the end is VDD
- Energy savings are huge is  $RC/T$  is small
- It is also necessary to recover energy and specific supply modules are requested

# RC charging at minimum dissipation theory

*IEEE TRANSACTIONS ON CIRCUITS AND SYSTEMS—I: FUNDAMENTAL THEORY AND APPLICATIONS, VOL. 47, NO. 7, JULY 2009*

*Optimal Charging of Capacitors*

*Steffen Paul, Student Member, IEEE, Andreas M. Schläffer, Student Member, IEEE, and Josef A. Nossek, Fellow, IEEE*

The input voltage for a given optimality criterion is computed by The methods used are variational calculus and Pontrjagin's maximum principle. This material is well established in mathematics and control and we refer to the literature for details [3]. The procedure to compute the input voltage  $v_i(t)$  is the following.

- 1) Given the dynamical system

$$\frac{dx}{dt} = a(x) + b(x)v(t)$$

with  $a, b, x$  scalars.

- 2) Define the Hamilton function

$$H(\lambda, x, v, t) = -L(x, v) + \lambda(a(x) + b(x)v(t)), \quad (1)$$

The time integral of  $-L(x, v)$  is to be minimized. For the case of loss minimization it measures the power in the resistor, in our case,  $L(x, v) = -(v_i(t) - v_C(t))^2/R$ . If minimal time charging is to be achieved, the function is simply one.

- 3) Solve

$$\frac{\partial H}{\partial v_i} = 0 \quad (2)$$

for  $v_i$ .

- 4) Solve

$$\frac{d\lambda}{dt} = -\frac{\partial H}{\partial x} \quad (3a)$$

$$\frac{dx}{dt} = \frac{\partial H}{\partial \lambda} \quad (3b)$$

$$H = \frac{(v_i(t) - v_C(t))^2}{R} + \lambda(t)\frac{1}{\tau}(v_i(t) - v_C(t)), \quad (7)$$



 
 


Fig. 3. Input signals for maximum efficiency of linear circuit.

 


Charge of  $C_L$

Logic state evaluation

 

 
Input voltage stable during transition  
otherwise non adiabatic dissipation



PMOS is on only if  $V_{DD}$  greater than  $V_T$   
Non adiabatic dissipation

$$\frac{1}{2} C_L V_T^2$$

# A more efficient solution

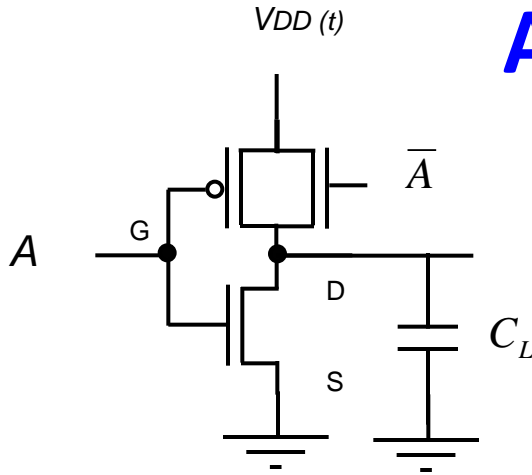


$$I_{Dn} = \frac{W_n}{L_n} \mu_n C'_{ox} [(V_{GSn} - V_{Tn})V_{DS} - V_{DS}^2]$$

$$I_{Dp} = \frac{W_p}{L_p} \mu_p C'_{ox} [(V_{SGp} - V_{Tp})V_{SD} - V_{SD}^2]$$

$$g_{on} = \frac{\partial I_{Dn}}{\partial V_{DS}} = \frac{W_n}{L_n} \mu_n C'_{ox} (V_{GSn} - V_{Tn}) = \frac{W_n}{L_n} \mu_n C'_{ox} (V_{DD} - V_{DD}(t) - V_{Tn})$$

$$g_{op} = \frac{\partial I_{Dp}}{\partial V_{DS}} = \frac{W_p}{L_p} \mu_p C'_{ox} (V_{GSn} - V_{Tn}) = \frac{W_p}{L_p} \mu_p C'_{ox} (V_{DD}(t) - V_{Tp})$$

$A=0$

 

$V_{DS}$  close to 0

we consider  $\frac{W_n}{L_n} \mu_n C'_{ox} = \frac{W_p}{L_p} \mu_p C'_{ox}$


$$g = \frac{W_n}{L_n} \mu_n C'_{ox} (V_{DD} - 2V_T)$$

W/L = 1    45 nm

1/g = 2500  $\Omega$

W/L = 10    45 nm

1/g = 250  $\Omega$

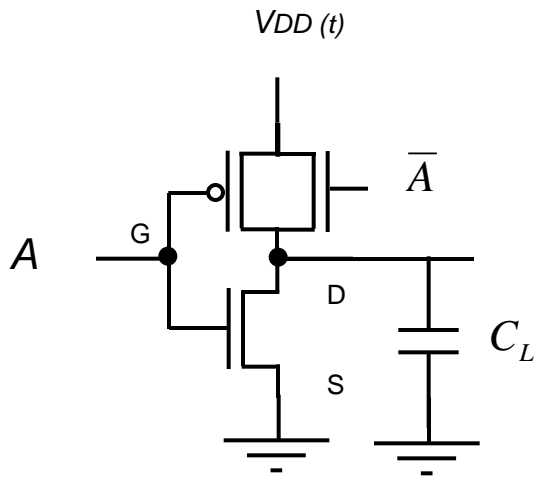

$$E_{dyn} = \frac{RC_L}{T} C_L V_{DD}^2 = \frac{L^2}{C_n} \frac{C_L^2}{\mu_n} \frac{V_{DD}^2}{(V_{DD} - 2V_T) T} \cdot 1$$

avec  $C_n = C'_{ox} WL$

With leakage power

$$E_{stat} = \frac{\mu_n C_n}{L^2} V_{th}^2 e^{-\frac{V_T}{nV_{th}}} V_{DD} T$$



avec  $V_{th} = \frac{kT}{e}$

$$n = 1 + \frac{C_D}{C_n}$$

$$E = a \frac{L^2}{C_n} \frac{C_L^2}{\mu_n} \frac{V_{DD}^2}{(V_{DD} - 2V_T) T} + \frac{\mu_n C_n}{L^2} V_{th}^2 e^{-\frac{V_T}{nV_{th}}} V_{DD} T$$

Activity factor = 1  
in adiabatic mode



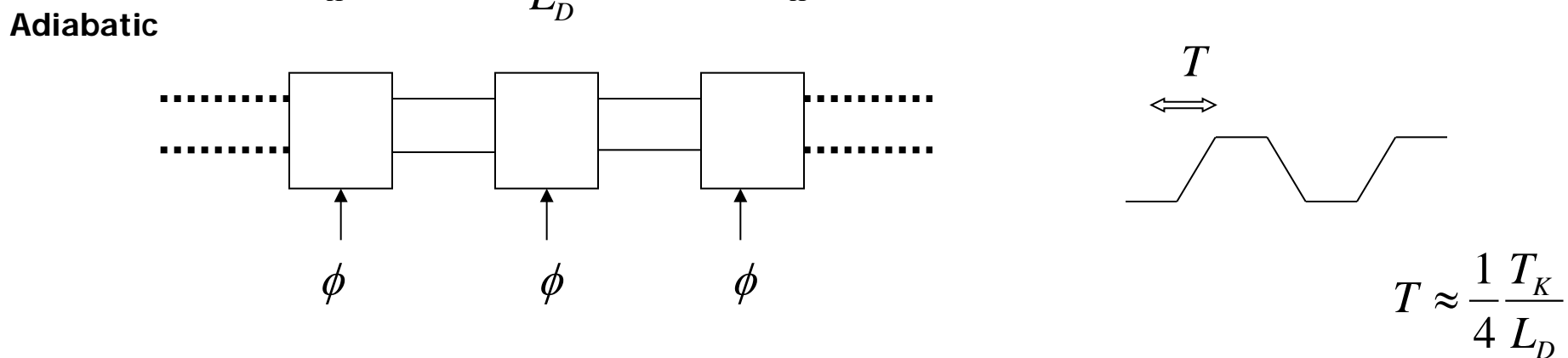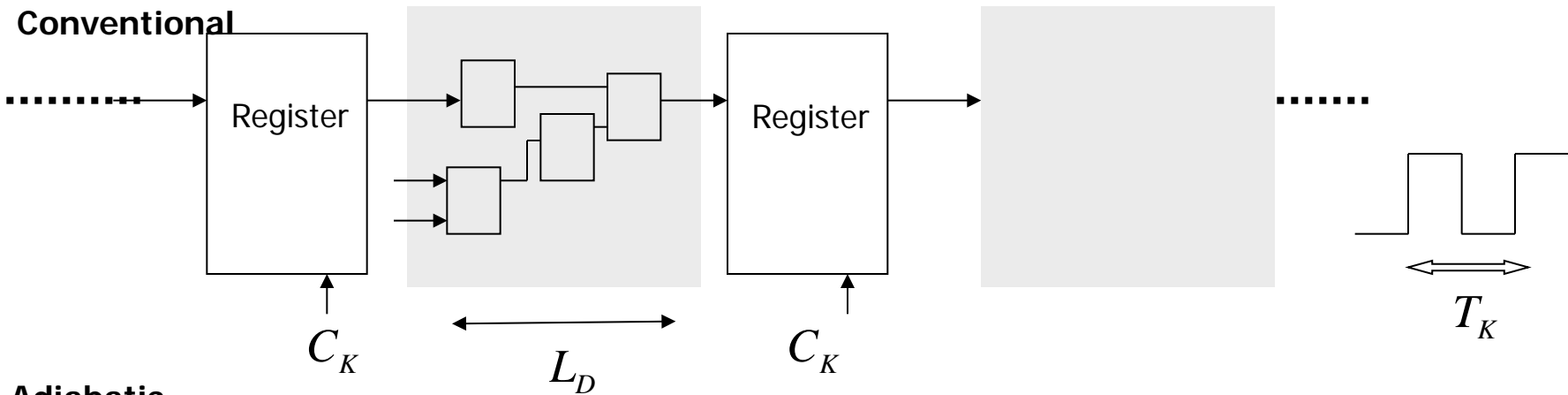

**Conventional**



$$E = \alpha \cdot \frac{1}{2} C_L V_{DD}^2 + \frac{\mu_n C_n}{L^2} V_{th}^2 e^{-\frac{V_T}{nV_{th}}} V_{DD} T_K$$

$$C_n = WLC'_{OX}$$

activity factor between 0.01 and 1

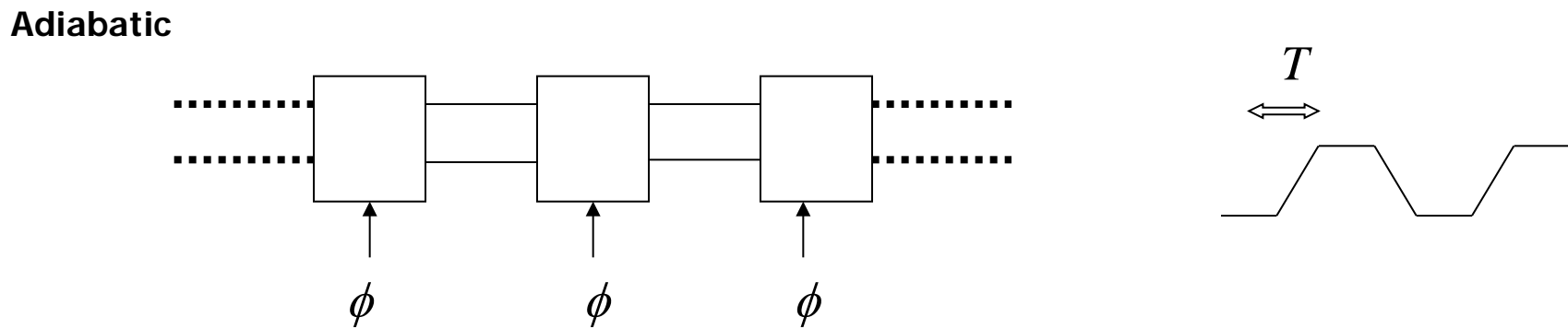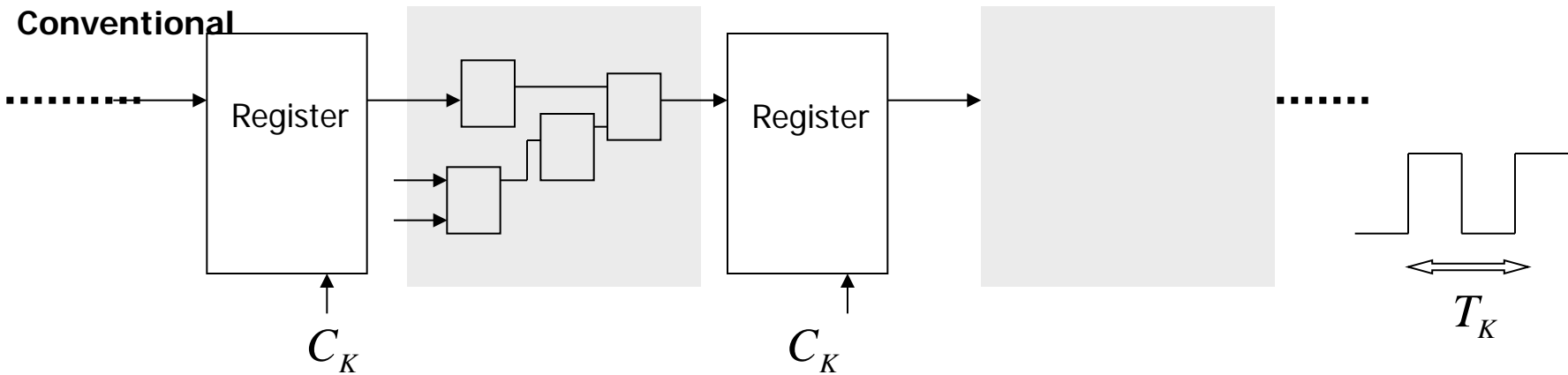**Adiabatic**

$$E = \frac{L^2 C_L^2}{C_n \mu_n} \frac{V_{DD}^2}{(V_{DD} - 2V_T) T} + \frac{\mu_n C_n}{L^2} V_{th}^2 e^{-\frac{V_T}{nV_{th}}} V_{DD} T$$



$$E_{opt} = \frac{L^2}{C_n} \frac{1}{\mu} \frac{C_L^2}{T} \cdot 8V_T$$

$$T_{opt} = \infty !!!$$


T optimum and E optimum

**Effect of  $V_T$**


**Without leakage**


**With leakage**
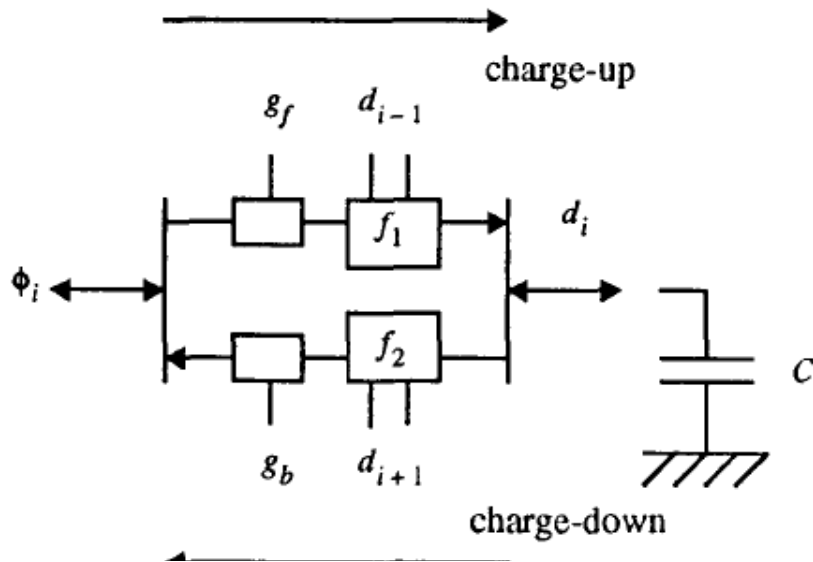
# From adiabatic logic to reversible logic



 
It is necessary to identify inputs from outputs, that is not possible with conventional logic but with reversible gates




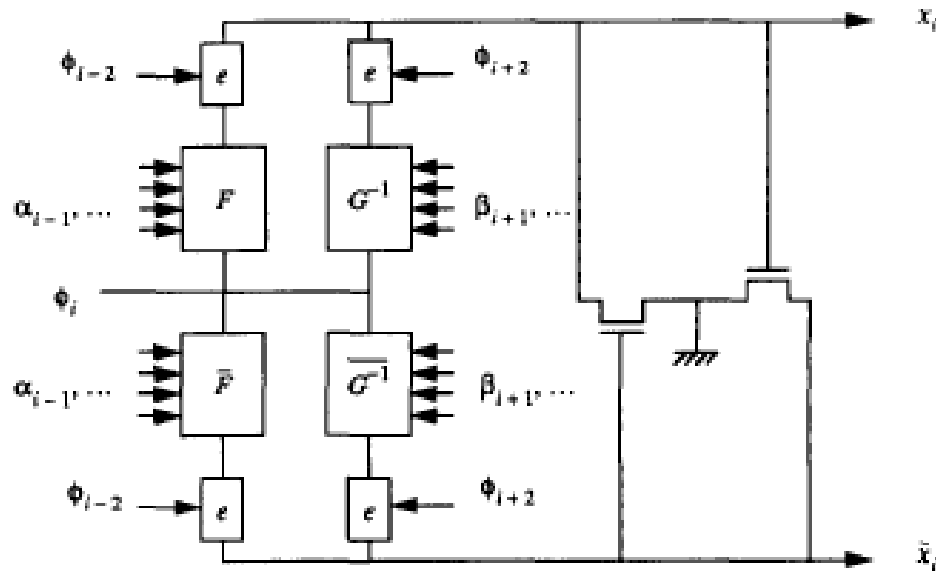

 
## The fully adiabatic pipeline

Fully adiabatic logic is complex but partially adiabatic logic is a good trade-off



# The quasi-adiabatic solution

  

Dissipated energy is not  $RC/T \cdot CV^2$

Dissipated energy is  $RC/T \cdot CV^2 + C \cdot Vt^2$


# Nanorelays for adiabatic logic

The threshold voltage is a limitation with CMOS technology and the subthreshold current a drawback

$$F = \frac{\epsilon_0 \cdot S \cdot V^2}{2(g - g_d)^2}$$

$$R = 2 \frac{4\rho\lambda}{3A} \quad A = \frac{F}{H\xi}$$
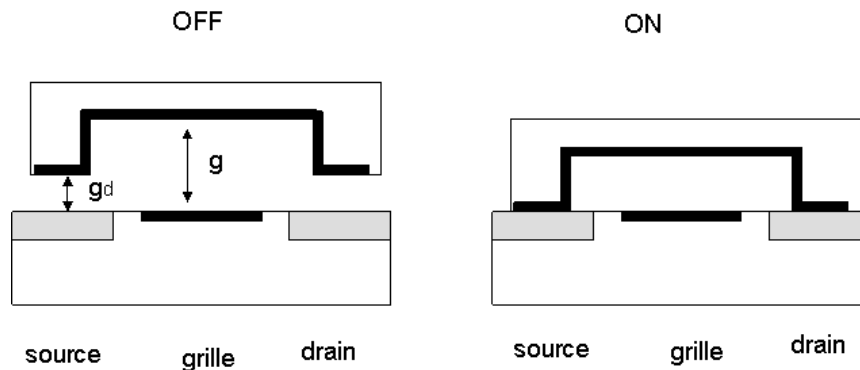
$$V_{PI} = \sqrt{\frac{8kg^3}{27\epsilon_0 WL}}$$



Leakage is zero

A voltage  $V_{PI}$  is necessary for contact

S electrostatic actuation surface

$\rho$  resistivity of the metal

$\lambda$  mean free path in metal

H hardness of metal

F electrostatic force

K effective spring constant of the beam


 


Fig. 15. The impact of scaling on contact resistance: (a) the total contact resistance and (b) contributions of Sharvin and Maxwell resistances to the total resistance.

with adiabatic logic

 

$$F = \frac{\varepsilon_0 \cdot S \cdot V^2}{2(g - g_d)^2}$$

$$R = 2 \frac{4\rho\lambda}{3A}$$

$$A = \frac{F}{H\xi}$$

$$E = \frac{32}{3} \frac{\rho\lambda H\xi}{\varepsilon_0 S} (g - g_d)^2 \frac{C_L^2}{T}$$

If we use this resistance model, energy does not depend on supply voltage !!



# Comparison MOS and nanorelays in adiabatic mode

$$E_{nems} = \frac{32}{3} \frac{\rho \lambda H \xi}{C_n} (g - g_d) \frac{C_L^2}{T}$$

$$E_{silicium} = \frac{18}{C_n} \frac{L^2}{\mu_n} \frac{C_L^2}{T} V_T$$

$$L = 2 \cdot 10^{-8}$$

$$\mu = 2 \cdot 10^{-2}$$

$$V_T = 0.1$$

$$\rho = 5 \cdot 10^{-8}$$

$$\lambda = 3 \cdot 10^{-8}$$

$$H = 10^9$$

$$\xi = 0.3$$

$$g - g_d = 10^{-8}$$




$$\eta = \frac{E_{nems}}{E_{cmos}} = \frac{10}{18} \frac{\rho \lambda H \xi}{L^2 V_T} (g - g_d)$$



$$\eta = 1.2$$

**Energies are not so different  
but models have to be  
confirmed**

**Zero leakage is the main  
advantage of nanorelays**

What kind of contact at nanoscale ?

 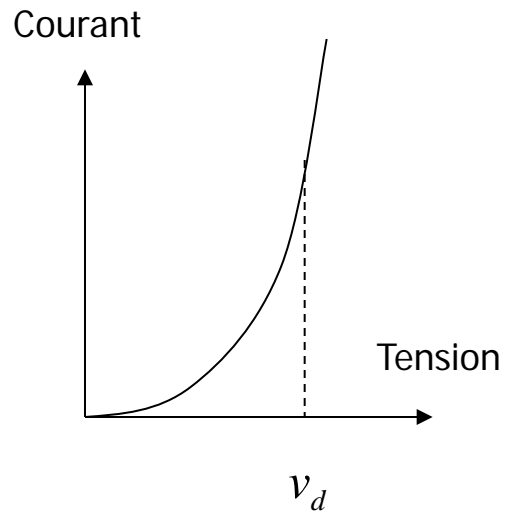 

  

$$E = \frac{32}{3} \frac{\rho \lambda H \xi}{\epsilon_0 S} (g - g_d)^2 \frac{C_L^2}{T} + C_L V_{DD} v_d$$

Non adiabatic dissipation

# Trade-off reliability-energy efficiency

## *Integrated Circuit Design with NEM Relays*

*Fred Chen<sup>2</sup>, Hei Kam<sup>1</sup>, Dejan Markovic<sup>3</sup>, Tsu-Jae King Liu<sup>1</sup>, Vladimir Stojanovic<sup>2</sup>, Elad Alon<sup>1</sup>*

*1Department of EECS, University of California, Berkeley, CA 94720, USA*

*2Department of EECS, Massachusetts Institute of Technology, Cambridge, MA 02139, USA*

*3EE Department, University of California, Los Angeles, CA 90095, USA*

The best-known contact material for minimum contact resistance is gold (Au), which has a hardness of 0.2-0.7GPa, a resistivity of 23nΩ·m, and an electron mean free path of 36 nm. **For the 90 nm equivalent devices used in our circuit study, the total contact resistance of a gold-based elastic-contact relay design is estimated to be on the order of 100 Ω even at a low  $V_{gb}$  of 0.3 V.**

Unfortunately, gold may not be suitable for fabrication of nanoscale features with fine pitch, and other more suitable materials are typically harder and hence have higher contact resistance. For example, if the physical contacts are instead formed with tungsten (W), which has a hardness of 1.1 GPa, resistivity of 55 nΩ·m, and electron mean free path of 33 nm, the estimated total contact resistance for an elastic contact at a  $V_{gb}$  of **0.3 V is ~1 kΩ**. In our circuit study we will present results for both the best-case (gold) and worst-case (tungsten) contact materials, including the reduction in contact resistance as a function of supply voltage.

# Conclusions

- Energy efficiency is the main nanoelectronic driver...
- Many improvements at circuit level
- New switches (Tunnel FET and NEMS) have to be confirmed for future ultra low power electronics but FDSOI and FinFETs are today solutions
- Adiabatic logic in association with new switches has to be investigated

# Bibliography

- **Low power electronics design**

Christian Piguet

CRC PRES

- **Proceedings of the IEEE**

February 2010 vol 98 Number 2

Circuit technology for ultra low power